 


VHDL multiplex 8 para 1

```
--  
-- Autor: George Maximo, Data: 01/10/2019 | versao 1.0.0  
--
```

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity multiplex8_to_1 is port  
(  
    A      : in std_logic_vector(7 downto 0);      --entradas  
    Sel    : in std_logic_vector(2 downto 0);      --selecao  
    X      : out std_logic  
);  
end multiplex8_to_1;  
  
architecture hardware of multiplex8_to_1 is  
begin  
    with Sel select  
        X <= A(0) when "000",  
        A(1) when "001",  
        A(2) when "010",  
        A(3) when "011",  
        A(4) when "100",  
        A(5) when "101",  
        A(6) when "110",  
        A(7) when "111";  
  
end hardware;
```



Saída waveforme mux 8 para 1:



```
-- VHDL demux 1 para 8
-- George Maximo de Sousa
```

```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity demux1_8 is port
```

```
(
    E      : in std_logic;
    X      : out std_logic_vector(7 downto 0);
    Sel    : in std_logic_vector(2 downto 0)
```

```
);
end demux1_8;
```

```
architecture hardware of demux1_8 is
```

```
begin
```

```
process(Sel, E)
```

```
begin
```

```
    case Sel is
```

```
        when "000" => X(0) <= E;
```

```
        when "001" => X(1) <= E;
```

```
        when "010" => X(2) <= E;
```

```
        when "011" => X(3) <= E;
```

```
        when "100" => X(4) <= E;
```

```
        when "101" => X(5) <= E;
```

```
        when "110" => X(6) <= E;
```

```
        when "111" => X(7) <= E;
```

```
    end case;
```

```
end process;
```

```
end hardware;
```

